

A unified approach to compact device modelling with the open source packages Qucs/ADMS and MAPP/Octave


Mike Brinson, Centre for Communications Technology, London Metropolitan University, UK,
mbrin72043@yahoo.co.uk.

- **Qucs-0.0.18: Structure and basic modelling features**
- **Qucs-0.0.19: Introducing the next generation Qucs simulation and modelling tools**
- **Qucs circuit simulation and device modelling: Simulation, subcircuits, post-simulation data processing, algebraic equation-defined components and embedded design routines**
- **Compact device modelling:** 1. **Equation-Defined Device models (EDD), Radio Frequency and Equation-Defined Models (FEDD)**
- **Compact device modelling:** 2. **Analogue Device Model Synthesis (ADMS) of Verilog-A behavioural and lower level device and circuit models; Qucs ADMS/Verilog-A “turn-key” tools**
- **Compact device modelling:** 3. **Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP)**
- **Qucs development:** A unified GPL compact device modelling and simulation platform
- **Summary**
- **References**

Presented at the IEEE EDS POLAND MINI-COLLOQUIUM - Training Course on Compact Modeling (TCCM), Torun Poland, 24 June 2015



 
Qucs-0.0.18: structure and basic modelling features



GPL software used by Qucs-0.0.18

- * ADMS – Automatic model synthesiser, <http://sourceforge.net/projects/mot-adms>
- ** PS2SP – PSPICE to SPICE preprocessor, <http://members.acon.at/fschmid7/>
- *** ASCO – SPICE circuit optimiser, <http://asco.sourceforge.net/>
- **** OCTAVE – Numerical analysis package, <https://www.gnu.org/software/octave/>

 Qucs-0.0.19: introducing the next generation Qucs simulation and modelling tools




* Berkeley Model and Algorithm Prototyping Platform (MAPP)

<http://draco.eecs.berkeley.edu:8765/jr/MAPP/wikis/home>



 Qucs circuit simulation and device modelling: Simulation



*Implementation : Qucs built-in; SPICE via RCL networks

Post-simulation data processing : 1. using Qucs

Equation blocks + simulation data sets → Data processing → Tables and plots

Constants: i, j, pi, e, kB, q

Immediate: 2.5, 1.4+j5.1, [1, 3, 4, 5, 7], [11, 12; 21, 22]

Ranges: Lo:Hi, :Hi, Lo:, :

Logical operators: !x, x&&y, x||y, x^^y, x?y:z, x==y, x!=y, x<y, x<=y, x>y, x>=y

Number suffixes: E, P, T, G, M, k, m, u, n, p, f, a


Matrices: M, M[2,3], M[:,3]

Arithmetic operators: +x, -x, x+y, x-y, x*y, x/y, x%y, x^y

abs adjoint angle arccos arccosec arccot arcosh arcoth arcsec arcsin arctan arg arsech arsinh artanh avg besseli0 besselj bessely ceil conj cos cosec cosech cosh cot coth cumavg cumprod cumsum dB dbm dbm2w deg2rad det dft diff erf erfc erfcinv erfinv exp eye fft fix floor Freq2Time GaCircle GpCircle hypot idft ifft imag integrate interpolate inverse kbd limexp linspace In log10 log2 logspace mag max min Mu Mu2 NoiseCircle norm phase PlotVs polar prod rad2deg random real rms Rollet round rtoswr rtoy rtoz runavg sec sech sign sin sinc sinh sqr sqrt srandom StabCircleL StabCircleS StabFactor StabMeasure stddev step stos stoy stoz sum tan tanh Time2Freq transpose unwrap variance vt w2dbm xvalue ytor ytos yvalue ztor ztos ztoy

transient simulation

 TR1
Type=lin
Start=0
Stop=10 ms
Points=500






Subcircuit

Equation



Eqn1
 $ts=(\max(\text{time})-\min(\text{time}))/\text{length}(\text{time})$
 $fs=1/ts$
 $Adft=dft(hg_sig.Vt)$
 $LAdft=\text{length}(hg_sig.Vt)$
 $Amp2=2*Adft[1:LAdft-1]$
 $LAdft02=LAdft/2$
 $Amp_squared=Adft[:LAdft02]*\text{conj}(Adft[:LAdft02])$
 $Amp=\sqrt{Amp_squared}$
 $f_bin=linspace(1, LAdft02, LAdft02)$
 $f=(f_bin-1)*fs/LAdft$
 $PLAmp=PlotVs(2*Amp/LAdft,f)$
 $PLPower=PlotVs(4*Amp*Amp/(LAdft*LAdft),f)$

* MATLAB, Mathworks, <http://www.mathworks.com/>
** Octave, <http://www.gnu.org/software/octave/>

   Limitations: NO user defined functions or control loops



  
Post-simulation data processing : 2. using Octave



% test RC transient simulation plus FFT of output.
clear;
Data = "RCFFTStem.dat";
qdset = loadQucsDataSet(Data);
[time] = getQucsVariable(qdset, "time");
[Vin_Vt] = getQucsVariable(qdset, "Vin.Vt");
[Vout_Vt] = getQucsVariable(qdset, "Vout.Vt");
[FTime] = getQucsVariable(qdset, "FTime");
showQucsDataSet(qdset);
[Y1 , Y2, freq] = plotFFT2V("Stem", "Frequency (Hz)", 0, 6000,
Vin_Vt, "Vin (V)", "black",
Vout_Vt, "Vout (V)", "red", 4, FTime);

RCFFTStem.m

 Algebraic equation-defined components and embedded design routines




```

Equation
Eqn1
is1=is
ic1=0.5*c2*pswrt
ic2=c1
VT=vt(300)
is2=is1*(1+vos/VT)
ib1=ib-0.5*ios
ib2=ib+0.5*ios
b1=ic1/ib1
b2=ic2/ib2
iee=c1/((b1+1)/ib1+((b2+1)/ib2))
gm1=c1/VT
rc1=1/(2*pi*gbp*c2)
rc2=rc1
re1=((b1+b2)/(2+b1+b2))*(rc1-1/gm1)
re2=re1
ree=valee
cee=(2*ic1/nswrt)-c2
dphi=90-pi
c1=0.5*c2*tan(dphi*pi/180)
gcm1=1/(cmrr*rc1)
ga=1/rc1
gb=(avol*rc1)/(r2*ro2)
ix=2*ic1*r2*gb-is1
temp1=(ro1*is1/VT)
isd1=ix*exp(temp1)+1e-32
temp2=ix/isd1
rc=VT*ln(temp2)/(100*ix)
gc=1/rc
vcc=abs(vcc)-vsp+VT*ln(iscp/is1)
ve=abs(vee)-vsn+VT*ln(iscn/is1)
rp=(vcc-vee)*(vcc-vee)/pd
    
```

Macromodel design equations


Macromodel parameters

 

SUB1
is=8e-16
vos=0.7e-3
c2=30e-12
r2=100e3
pswrt=0.625e6
nswrt=0.5e6
ios=20e-9
ib=80e-9
gbp=1e6
va=200
pm=70
cmrr=31622.8
avol=200e3
vsp=14.2
vsn=-13.5
vcc=15
vee=-15
iscp=25e-3
iscn=25e-3

**Circuit
design
equations**

**Filter
specification**




 


Equation
Eqn1
Q=f0/bw
r1=r3/(2*h0)
c1=1/(pi^2*bw)
r2=r3/(4*Q^2-2*h0)

dc simulation
DC1


ac simulation
AC1
Type=lin
Start=800Hz
Stop=1200Hz
Points=21

    Parameter sweep
SW1
Sim=AC1
Type=lin
Param=bandwidth
Start=100
Stop=400
Points=10






Compact Device Modelling 1: Subcircuits and EDD models

Photodiode subcircuit body

 


PD
File=name
Cj0=60p
Is=0.34p
N=1.35
Bv=60
Tt=10n
Responsivity=0.5
Rseries=1m
Rsh=1M

Test circuit and simulation data

   

Green denotes light source and light bus

 Compact Device Modelling 1: EDD specifications



$$I = I(V)$$

$$g = \frac{dI}{dV}$$

$$Q = Q(V, I)$$

$$c = \frac{dQ}{dV}$$

$$C = \frac{dQ(V)}{dV} + \frac{dQ(I)}{dV}$$

- EDD is a multi-terminal non-linear component with branch currents that can be functions of EDD branch voltage, and stored charge that can be a function of both EDD branch voltages and Currents.
- EDD is similar, but more advanced to the SPICE 3f5 B type controlled sources.
- EDD can be combined with conventional circuit components and Qucs equation blocks when constructing compact device models and subcircuit macromodels.
- EDD is an advanced component, allowing users to construct prototype experimental models from a set of equations derived from physical device properties.



Compact Device Modelling 1: EDD Photo-diode model

D1

```
I1=(V1>-5.0*N*Vt_T2) ? Area*Is_T2*(limexp(V1/(N*Vt_T2))-1.0)+V1*GMIN : 0
Q1=(V1 < Fc*Vj) ? Tt*I1+Area*(Cj0_T2*Vj_T2/(1-M))*(1-(1-V1/Vj_T2)^(1-M)) : 0
I2=(-Bv<V1) && (V1<-5.0*N*Vt_T2) ? -Area*Is_T2+V1*GMIN : 0
Q2=(V1 >= Fc*Vj) ? Tt*I1+Area*Cj0_T2*(F1+(1/F2)*(F3*(V1-Fc*Vj_T2)+(M/(2*Vj_T2))*(V1*V1-Fc*Fc*Vj_T2*Vj_T2))) : 0
I3=(V1===-Bv) ? -lbv : 0
Q3=0
I4=(V1<-Bv) ? -Area*Is_T2*(limexp(-(Bv+V1)/Vt_T2)-1.0+Bv/Vt_T2) : 0
Q4=0
```

I5=V5/(Rsh+1e-20)


Q5=0

I6=-Responsivity*V7


Q6=0

I7=0

Q7=0

 

 PD1
N=1.35
Is=0.34p
Bv=60
Ibv=1e-3
Vj=1.0
Cj0=60p
M=0.5
Area=1
Fc=0.5
Tt=10n
Xti=3.0
Tnom=26.85
Temp=26.85
Eg=1.16
Responsivity=0.5
Rsh=1M
Rseries=1m
Rs=0.01



Equation

Eqn2

$$Cj0_T2=Cj0*(1+M*(400e-6*(T2-T1)-(Vj_T2-Vj)/Vj))$$

$$Vt_T2=(kB*T2/q)$$

$$rs_AREA=Rs/AREA$$

$$GMIN=1e-12$$

$$A=7.02e-4$$

$$B=1108$$

$$T1=Tnom+273.15$$

$$Vj_T2=(T2/T1)*Vj-(2*kB*T2/q)*ln((T2/T1)^{1.5})-((T2/T1)*Eg_T1-Eg_T2)$$

$$Is_T2=Is*(T2/T1)^(Xti/N)*limexp((-q*Eg_T1)/(kB*T2)*(1-T2/T1))$$

$$Eg_T1=Eg-A*T1*T1/(B+T1)$$

$$Eg_T2=Eg-A*T2*T2/(B+T2)$$

$$T2=Temp+273.15$$


Equation

Eqn3

$$F1=(Vj/(1-M))*(1-(1-Fc)^{(1-M)})$$

$$F2=(1-Fc)^{(1+M)}$$


$$F3=1-Fc^{(1+M)}$$

 

Compact Device Modelling 1: EDD photo-transistor model

Schematic symbol, default parameter list and equivalent circuit of an npn bipolar photo-transistor

 The phototransistor consists of an Ebors-Moll bipolar junction transistor model which has been extended to include depletion and diffusion capacitance, forward and reverse Early effects, high current forward and reverse beta degradation, thermal and shot noise, plus a light bus which connects external light signals to the phototransistor.



Ptran1
Bf=100
Br=0.1
ls=1e-10
Nf=1
Nr=1
Var=100
Vaf=100
Mje=0.33
Vje=0.75
Cje=1p
Mjc=0.33
Vjc=0.75
Cjc=2p
Tr=100n
Tf=0.1n
Ikf=0.5
Ikr=0.5
Rc=2
Re=1
Rb=100
Kf=1e-12
Ffe=1.0
Af=1.0
Responsivity=1.5
P0=2.6122e3
P1=-1.4893e1
P2=3.0332e-2
P3=-2.5708e-5
P4=7.6923e-9

Compact Device Modelling 1: Photo-transistor specification

Model parameters

Name	Symbol	Description	Unit	Default
BF	β_f	Forward beta		100
BR	β_r	Reverse beta		0.1
Is	I_s	Saturation current	A	1e-10
Nf	N_f	Forward emission coefficient		1
Nr	N_r	Reverse emission coefficient		1
Var	V_{ar}	Reverse Early voltage	V	100
Vaf	V_{af}	Forward Early voltage	V	100
Mje	M_{je}	Base-emitter exponential factor		0.33
Vje	V_{je}	Base-emitter built-in potential	V	0.75
Cje	C_{je}	Base-emitter zero-bias depletion capacitance	F	1p
Mjc	M_{jc}	Base-collector exponential factor		0.33
Vjc	V_{jc}	Base-collector built-in potential	V	0.75
Cjc	C_{jc}	Base-collector zero-bias depletion capacitance	F	1p
Tr	T_r	Ideal reverse transit time	s	100n
Tf	T_f	Ideal forward transit time	s	0.1n
Ikf	I_{kf}	High current corner for forward beta	A	0.5
Ikf	I_{kr}	High current corner for reverse beta	A	0.5
Rc	R_c	Collector series resistance	Ω	2
Re	R_e	Emitter series resistance	Ω	1
Rb	R_b	Base series resistance	Ω	100
Kf	K_f	Flicker noise coefficient		1e-12
Ffe	F_{fe}	Flicker noise frequency exponent		1
Af	A_f	Flicker noise exponent		1
Responsivity	$Responsivity$	Responsivity at peak wavelength	A/W	1.5
P0	P_0	Relative selectivity polynomial coefficient	%	2.6122×10^3
P1	P_1	Relative selectivity polynomial coefficient	%/nm	-1.4893×10^1
P2	P_2	Relative selectivity polynomial coefficient	%/nm ²	3.0332×10^{-2}
P3	P_3	Relative selectivity polynomial coefficient	%/nm ³	-2.5708×10^{-5}
P4	P_4	Relative selectivity polynomial coefficient	%/nm ⁴	7.6923×10^{-9}

Compact Device Modelling 1: Photo-transistor model equations

DC I/V characteristics {

$$IEC = Is \cdot \left[\exp\left(\frac{V(BI, CI)}{Nr \cdot vt(300)}\right) - 1 \right]$$

$$IDC2 = \frac{IEC}{\beta r} + GMIN \cdot V(BI, CI)$$

$$IDE2 = \frac{ICC}{\beta f} + GMIN \cdot V(BI, EI)$$

$$ICC = Is \cdot \left[\exp\left(\frac{V(BI, EI)}{Nf \cdot vt(300)}\right) - 1 \right]$$

$$ICT = \frac{[ICC - IEC]}{\left(\frac{q1}{2}\right) \cdot (1 + \sqrt{1 + 4 \cdot q2})}$$

$$q1 = 1 + \frac{V(BI, CI)}{Vaf} + \frac{V(BI, EI)}{Var}$$

$$q2 = \frac{ICC}{Ikf} + \frac{IEC}{Ikr}$$

$$vt(T) = \frac{K \cdot T}{q}$$

Capacitance {

$$CBC = \frac{dQ(BI, CI)}{dV(BI, CI)} = \frac{Cjc}{\left[1 - \frac{V(BI, CI)}{Vjc}\right]^{Mjc}} + Tr \cdot \frac{dIEC}{dV(BI, CI)}$$

$$= 2^{Mjc} \cdot Cjc \cdot \left[\frac{2 \cdot Mjc \cdot V(BI, CI)}{Vjc} + (1 - Mjc) \right] + Tr \cdot \frac{dIEC}{dV(BI, CI)}$$

$$CBE = \frac{dQ(BI, EI)}{dV(BI, EI)} = \frac{Cje}{\left[1 - \frac{V(BI, EI)}{Vje}\right]^{Mje}} + Tr \cdot \frac{dICC}{dV(BI, EI)}$$

$$= 2^{Mje} \cdot Cje \cdot \left[\frac{2 \cdot Mje \cdot V(BI, EI)}{Vje} + (1 - Mje) \right] + Tr \cdot \frac{dICC}{dV(BI, EI)}$$

Photo current {

$$Iopt = Gpbc \cdot Popt$$

$$Gpbc = \frac{\text{RelSensitivity} \cdot \text{Responsivity}}{\beta f \cdot 100}$$

$$\text{RelSensitivity} = P0 + P1 \cdot \lambda + P2 \cdot \lambda^2 + P3 \cdot \lambda^3 + P4 \cdot \lambda^4$$

Noise {

$$iRcn^2 = \frac{4 \cdot K \cdot T}{Rc} \cdot \Delta f$$

$$iRen^2 = \frac{4 \cdot K \cdot T}{Re} \cdot \Delta f$$

$$iICTsn^2 = 2 \cdot q \cdot IC \cdot \Delta f$$

$$iRban^2 = \frac{8 \cdot K \cdot T}{Rb} \cdot \Delta f$$

$$iRbbn^2 = \frac{8 \cdot K \cdot T}{Rb} \cdot \Delta f$$


$$ibsn^2 = 2 \cdot q \cdot IB \cdot \Delta f$$

$$ibfn^2 = Kf \cdot \frac{IB^{Af}}{f^{Ffe}} \cdot \Delta f$$

Where K is the Boltzmann constant, T is the temperature in Kelvin, q is the electron charge, GMIN is a small admittance in parallel with the device junctions, Δf is the noise frequency bandwidth in Hz and λ is the light wavelength in nm. Other symbols and node names are defined in the previous slides.

Compact Device Modelling 1: Basic npn transistor model

Equation defined device

 


$$I=I(V), g=\frac{dI}{dV}$$


$$Q=Q(I,V)$$

$$C = \frac{dQ}{dV} = \frac{dQ(V)}{dV} + \frac{dQ(I)}{dI} \cdot g$$

Large signal DC model

 


Generated symbol

 


SUB
File=name

Redrawn symbol

 

PTran
File=name
Bf=100
Br=0.1
ls=1e-10
Nf=1
Nr=1
Var=100
Vaf=100
Rc=2
Rb=100
Re=1
lkf=0.5
lkr=0.5

 Compact Device Modelling 1: DC simulation test



dc simulation



DC1

Parameter sweep

SW1
Sim=SW2
Type=log
Param=lb
Start=1e-6
Stop=1m
Points=16

Parameter sweep

  SW2
Sim=DC1
Type=lin
Param=Vce
Start=0
Stop=5
Points=51



Compact Device Modelling 1: Adding capacitance to the phototransistor model


Charge equations

$$Q(BI, CI) = \int_0^{V(BI, CI)} CBC \cdot dV = Tr \cdot IEC + 2^{Mjc} \cdot Cjc \cdot \left[Mjc \cdot \frac{V(BI, CI)^2}{Vjc} + (1 - Mjc) \cdot V(BI, CI) \right] \quad \forall V(BI, CI) > \frac{Vjc}{2}$$

$$= Tr \cdot IEC + \frac{Cjc \cdot Vjc}{1 - Mjc} \left[1 - \left(1 - \frac{V(BI, CI)}{Vjc} \right)^{1 - Mjc} \right] \quad \forall V(BI, CI) \leq \frac{Vjc}{2}$$

$$Q(BI, EI) = \int_0^{V(BI, EI)} CBE \cdot dV = Tf \cdot ICC + 2^{Mje} \cdot Cje \cdot \left[Mje \cdot \frac{V(BI, EI)^2}{Vje} + (1 - Mje) \cdot V(BI, EI) \right] \quad \forall V(BI, EI) > \frac{Vje}{2}$$
 
$$= Tf \cdot ICC + \frac{Cje \cdot Vje}{1 - Mje} \left[1 - \left(1 - \frac{V(BI, EI)}{Vje} \right)^{1 - Mje} \right] \quad \forall V(BI, EI) \leq \frac{Vje}{2}$$



PTran

File=name

Bf=100

Br=0.1

Is=1e-10

Nf=1

Nr=1

Var=100

Vaf=100

Rc=2

Rb=100

Re=1

Ikf=0.5

Ikr=0.5

Mje=0.33

Vje=0.75

Cje=1p

Mjc=0.33


Vjc=0.75

Cjc=2p

Tr=100n


Tf=0.1n

EDD blocks

 

Compact Device Modelling 1: Simulating capacitance effects

AC gain

 

Parameter sweep

SW1
Sim=AC1
Type=list
Param=lb
Values=[50u; 200u; 500u]

dc simulation



DC1

Equation


Eqn1
 $\text{AC_beta} = I_c / I_{base,i}$

ac simulation

  AC1
Type=log
Start=1 kHz
Stop=10 GHz
Points=101
acfrequency: 7.76e+04
 $I_b: 5e-05$
 $\text{AC_beta}: 110-j3.44$



C_{be} and R_{be} extraction

 

PTran1

Bf=100

Br=0.1

Is=1e-10

Nf=1

Nr=1

Var=100

Vaf=100

Rc=2

Rb=100

Re=1

Ikf=0.5

Ikf=0.5

Mje=0.33

Vje=0.75

Cje=1p

Mjc=0.33

Vjc=0.75

Cjc=2p

Tr=100n

Tf=0.1n

Parameter sweep

SW1

Sim=SP1

Type=lin

Param=Vbe

Start=-1

Stop=0.5


Points=71

S parameter simulation

SP1

Type=const

Values=[100kHz]

 

dc simulation

DC1

Equation

Eqn1

$y = \text{stoy}(S)$

$PL_y11 = \text{PlotVs}(y[1,1], Vbe)$



$Cbe = \text{imag}(y[1,1]) / \Omega$

$Rbe = 1 / \text{real}(y[1,1])$

$PL_Cbe = \text{PlotVs}(Cbe, Vbe)$


$PL_Rbe = \text{PlotVs}(Rbe, Vbe)$

$\Omega = 2 * \pi * \text{frequency}$

  

Compact Device Modelling 1: Adding photo-electric effects

 Si photo-transistor relative sensitivity data




Measured data


Wavelength (nm)	Relative reponsivity (%)
500	15
550	25
600	40
650	58
700	77
750	95
800	100
850	95
900	80
950	65
1000	35

Curve fitting program

```
## Simple phototransistor responsivity fitting
## program - works with Octave or MATLAB
data = load('data.dat');
Ldata = data(:,1);
Sdata = data(:,2);
## Fit polynomial
Order = 4;
p = polyfit(Ldata, Sdata, Order);
## Evaluate the fitted polynomial
x=linspace(min(Ldata), max(Ldata), 101);
y = polyval(p,x);
## Plot
plot(x,y, ' ', Ldata, Sdata,'x');
legend('Fitted polynomial', 'Original data');
```

 

EDD light bus model

 

Compact Device Modelling 1: Qucs Radio Frequency Defined Device (RFDD)

- Qucs RFEDD is a frequency dependent equation defined device based on two-port and multi-port electrical network structures.
- Two-port RFEDD are similar in structure to the well-known two-port networks commonly employed in the linear analysis of amplifiers and filters.
- Multi-port RFEDD allow, for example, modelling of directional couplers, isolators and other multi-port high frequency devices.
- Admittance (Y), impedance (Z), scattering (S), hybrid (H), inverse hybrid (G), transmission (A) and scattering transmission (T) two-port devices are implemented
In contrast to the two-port device, the multi-port RFEDD can only be defined for Y, Z or S Networks.
- Qucs RFEDD parameters are numerical or algebraic complex numbers. The latter can be functions of numerical constants, variables from Qucs equation blocks, subcircuit Parameters, mathematical operators and functions defined in the Verilog-A HDL and the Qucs function library.
- The real and imaginary parts of RFEDD parameters may also be functions of small signal simulation frequency (F) or operator S ($S = j \cdot \omega = j \cdot 2 \cdot \pi \cdot F$).


Compact Device Modelling 1: RFDD high frequency inductance

Equations and model

$$Rv1 = K1 \cdot \sqrt{F}, \quad Rv2 = K2 \cdot \sqrt{F}$$

$$Lv = [K3 - K4 \cdot \ln(K5 \cdot F)] \cdot 1e-6$$

Where $K1, K2, K3, K4$ and $K5$ are constants:

 


RF1

$$[A] = \begin{bmatrix} P11 & P12 \\ P21 & P22 \end{bmatrix} = \begin{bmatrix} 1 & Z(\text{real}) + j \cdot Z(\text{imag}) \\ 0 & 1 \end{bmatrix}$$


Qucs RFEDD model



 COIL1
R1=6200
R2=1.59
K1=1.49e-5
K2=0.268
K3=1.19
K4=1.4e-2
K5=6.9e-6
C1=0.139e-12






Simulation results



 


Compact Device Modelling 1: RFDD high frequency skin effect noise

   
Noise model: standard plus RFEDD non-linear components



   Noise model: Verilog-A block plus RFEDD non-linear components



 
Compact Device Modelling 3: Verilog-A model generation



Compact Device Modelling 3: Route for generating Verilog-A compact device models

The following diagram illustrates the initial stage in the construction of a Qucs Verilog-A compact device model

Qucs subcircuit symbol

 

name

Param1 = Value1

Param2 = Value2

Param3 = value3

"
"
"
"

Qucs subcircuit structure

- 1 Current equation blocks
- 2 Charge equation blocks
- 3 Model initialisation block
- 4 Standard and noise free resistors
- 5 Parameter blocks
- 6 Voltage controlled current blocks
- 7 Current to voltage conversion blocks
- 7 Shot noise current blocks
- 8 Flicker noise current blocks



Verilog-A code template

```
// Code structure
`include "disciplines.vams"
`include "constants.vams"
module name (P1, P2, P3, .... Pn);
inout P1, P2, P3, ..... Pn ;
electrical P1, P2, P3, ..... Pn ;
// Definition of local internal nodes
// Parameter values and descriptions
// Definition of variables and quantities
analog begin
// Model initialisation code
// Model quantity equations
// Current contributions
// Noise contributions
end
module end
```

Compact Device Modelling 3: Qucs EDD to Verilog-A code

Relationships between Qucs schematic symbols and Verilog-A code fragments

Fundamental EDD blocks

  Qucs symbol	Quantity equations	Verilog-A code fragment	Quantity equations	Verilog-A code fragment
	<p>Iname = I1 = f(V2, V3, V8)</p> <p>I2, I3, I8 = 0 and Q1, Q2, Q8 = 0.</p> <p>Where $V_m = V(n_{xm}, n_{ym})$ or $V_m = V(n_{xm})$, and $2 \leq m \leq 8$.</p>	<p>Iname = f(V2, V3, V8);</p> <p>Or</p> <p>Iname <+ f(V2, V3, V8);</p>	<p>(a) Model initialisation block</p> <p>Equation</p> <p>Eqn1</p> <p>con1=</p> <p>con2=</p> <p>con3=</p>	<p>@(initial_model)</p> <pre>begin con1 =; con2 =; con3 =; end</pre>
	<p>Q1 = f(V1, V2, V8, I1, I2, I8)</p> <p>Q2, Q8 = 0.</p> <p>Where $V_m = V(n_{xm}, n_{ym})$ or $V_m = V(n_{xm})$, and $1 \leq m \leq 8$.</p>	<p>I(nx1, ny1) <+ ddt(Q1);</p> <p>Or</p> <p>I(nx1, ny1) = ddt(Q1);</p>	<p>(b) Standard resistors</p> <p>n_x — R — n_y</p> <p>R=R</p>	<p>I(nx, ny) <+ V(nx, ny)/R;</p> <p>I(nx, ny) <+ white.noise((FourKT/R, "thermal");</p> <p>Where $\text{FourKT} = 4.0 \cdot \text{'P_K} \cdot \\temperature, and $\text{'P_K} = 1.3806505e-23 \text{ K}^{-1}$, $\\$temperature$ is the resistor temperature in Kelvin.</p>
			<p>(c) Noise free resistors</p> <p>I1 = V1/R = V(nx, ny)/R</p>	<p>I(nx, ny) <+ V(nx, ny)/R;</p>
			<p>(d) Voltage controlled current block</p> <p>n_x — G=X — n_y</p> <p>Iname = X * V(nx, ny)</p>	<p>Iname = X * V(nx, ny);</p>
			<p>(e) current to voltage conversion block</p> <p>n_x — 1 — n_y</p> <p>Iname = I1 = V1</p>	<p>Iname = V(nx);</p>

Compact Device Modelling 3: The Qucs/“Analog Device Model Synthesiser” Verilog-A subset

The “Analog Device Model Synthesiser” (ADMS) software is supplied with little documentation!

These brief notes provide a basic introduction to the Qucs/ADMS Verilog-A subset

- Verilog-A is a case sensitive language.
- Comments: (1) single line comments start with `//`,
(2) block comments begin with `/*` and end with `*/`
- Identifiers are sequences of letters, digits, dollar signs '\$' and the underscore '_'; the first letter of an identifier must not be a digit.
- Qucs/ADMS version 2.34 keywords: **parameter, aliasparameter, aliasparam, module, endmodule, function, endfunction, discipline, potential, flow, domain, ground, enddiscipline, nature, endnature, input, output, inout, branch, analog, begin, end, if, while, case, endcase, default, for, else, integer, real, string, from, exclude, inf, INF.**
- Compiler directives: ``define, `undef, `ifdef, `else, `endif, `include.`
- Data types: **integers, reals and strings.**
- Predefined constants in “constants.vams”: ``M_PI, `M_TWO_PI, `M_PI_2, `M_PI_4, `M_1_PI, `M_2_PI, `M_2_SQRTPI, `M_E, `M_LOG2E, `M_LOG10E, `M_LN2, `M_LN10, `M_SQRT2, `M_SQRT1_2, `P_Q, `P_C, `P_K, `P_H, `P_EPS0, `P_U0, `P_CELSIUS0.`
- Variables are named objects that contain a value of a particular type. They are initialised to zero or unknown. They retain their value until changed by an assignment statement.



Compact Device Modelling 3: The Qucs/“Analog Device Model Synthesiser” Verilog-A subset continued

- Parameters are declared with statements of the form:
**parameter integer size=16; parameter real period = 1.0 from (0:inf);
parameter integer dir = 1 from [-1:1] exclude 0;**
- Verilog-A natures and disciplines are listed in file “disciplines.vams”
- Port, net and node examples in Verilog-A:
**module amp(out1, in1);
 input in1;
 output out1;
 electrical out1, in1;**
- Branches are declared with statement **branch (n1,n2) b1;**
- Signal access function examples: **V(n2), I(n), V(b1), I(b1), V(n,m), I(n,m)**
- Current contribution examples:
**I(diode) <+ Is*(limexp(V(diode)/\$vt)-1);
I(diode) <+ ddt(-2*cj0*phi*sqrt(1-V(diode)/phi));**
- Qucs/ADMS allows an extensive range of Verilog-AMS operators and mathematical functions.
- Environmental Functions: **\$temperature, \$vt, \$strobe, \$finish, \$given, \$parameter_given.**
- Analogue operators: **@(initial_step), @(final_step), @(initial_model), @(initial_instance).**

Compact Device Modelling 3: The Qucs/“Analog Device Model Synthesiser” Verilog-A subset continued

Analogue behavioural statements:

1. Analog process/procedural block;

```
analog begin
```

```
    I(diode) <+ Is*(limexp(V(diode)/$vt)-1);
```

```
    qd      = tf*I(diode) -2*cj0*phi*sqrt(1-V(diode)/phi);
```

```
    I(diode) <+ ddt(qd);
```

```
end
```

2. Assignment statements consist of a variable followed by = and an expression

3. Conditional operator cond ? Val1 : Val2, for example

```
State = (V(d) > 0.0) ? 1 : -1;
```

TRUE = non-zero value

4. if-else statement:

```
If (V(ps,ns) > thresh)
```

```
    I(p,n) <+ 1;
```

```
else
```

```
    I(p,n) <+ 0;
```

5. Case statement:

```
case (select)
```

```
0 : out = I(in0);
```

```
1 : out = I(in1);
```

```
2 : out = I(in2);
```

```
default : out = 0;
```

```
endcase
```

6. While statement:

```
test = 4;
```

```
While( test) begin
```

```
    A = A+1;
```

```
    B = B-1;
```

```
    test = test-1;
```

```
end
```

7. For loops:

```
for (i=0; i <10; i=i+1) begin
```

```
..
```

```
end
```

8. User defined functions
and function calls:



More details of Qucs/ADMS Verilog-A statement coverage is given in:

http://www.mos-ak.org/london_2014/presentations/09_Mike_Brinson_MOS-AK_London_2014.pdf

Compact Device Modelling 3: The Qucs/“Analog Device Model Synthesiser” Verilog-A subset; special features and problems

- Although Verilog-A is standardised, published versions of ADMS implement different subsets of verilog-A.
- Simulator interface facilities may vary: for example **\$strobe** is replaced/added to by **\$error** and **\$warning** in QucsStudio.
- The inclusion mechanism for Verilog-A predefined constants, natures and disciplines files can change from simulator to simulator: for example use of **`include constants.h** and **`include disciplines.h** by SymicaDE.
- Parameter statement descriptive elements vary significantly among circuit simulator implementations: for example Qucs and QucsStudio use **`attr(info = “description”)**, or **`attr(desc=“description”)** and **unit=“value”** other simulators use **`P(.....)**.
- Verilog-A compact modelling extensions: special features tailored to compact device modelling have been added to the MOT-ADMS 2.30 software, including **desc**, **unit**, **\$parameter_given**, **\$given**, **aliasparameter** and **string** type in **parameters**. In addition the function **ddx** is now adopted in the language standard, where **ddx** takes a variable and a node potential (for example **gm = ddx(Ids,V(g));**) and returns the symbolic partial derivative of the variable with respect to the node potential, holding all other potentials constant. Qucs and QucsStudio implement these extensions but other circuit simulators may not.
- Each circuit simulator uses one or more backend XML script files for C++ code generation and model interfacing to the main body of C++ code: as these XML scripts are specific to each simulator API there are likely to be differences in the C++ model generated. One example being electrical noise: Verilog-A statements **white_noise(pwr, <name>)**, **flicker_noise(pwr, <exp>,<name>)** are implemented in Qucs and QucsStudio but not, for example, in ngspice.
- In addition to the above are the results from new types of circuit simulation, like for example
- Harmonic Balance, correct or not?

Compact Device Modelling 3: Building a Qucs EDD/Verilog-A model; part 1 – DC characteristics

EPFL-EKV v2.6 long channel nMOS equations

$$Vg = V(gate) - V(bulk), \quad Vs = V(source) - V(bulk), \quad Vd = V(drain) - V(bulk)$$


$$VGprime = Vg - VTO + PHI + GAMMA \cdot \sqrt{PHI}$$

$$VP = VGprime - PHI - GAMMA \cdot \left[\sqrt{VGprime + \left(\frac{GAMMA}{2} \right)^2} - \frac{GAMMA}{2} \right]$$

$$n = 1 + \frac{GAMMA}{2} \cdot \sqrt{VP + PHI + 4 \cdot Vt}, \quad BETA = KP \cdot \frac{W}{L} \cdot \frac{1}{1 + THETA \cdot VP}$$


$$X1 = \frac{Vp - Vs}{Vt}, \quad If = [\ln(1 + \text{limexp}(X1/2))]^2, \quad X2 = \frac{Vp - Vd}{Vt}, \quad Ir = [\ln(1 + \text{limexp}(X2/2))]^2$$
 
$$Ispecific = 2 \cdot n \cdot BETA \cdot vt^2, \quad Ids = Ispecific \cdot (If - Ir)$$



Model

Symbol

 

EKVL

File=name

L=10e-6

W=10e-6

VTO=0.5


GAMMA=0.7

PHI=0.5

KP=50e-6

THETA=50e-3

Temp=26.85

 

drain
source
bulk
Equation
Eqn1
 $T2=Temp+173.15$

drain
source
source
drain
Ispecific
If
Ir
D10
 $I1=V2*(V3-V4)$
 $I2=V2$
 $I3=V3$
 $I4=V4$

Compact Device Modelling 3: Building a Qucs EDD/Verilog-A model; part 2 – intrinsic charge characteristics

EPFL-EKV v2.6 long channel nMOS equations → Symbol

$$nq = 1 + \frac{GAMMA}{2 \cdot \sqrt{VP + PHI + 1e-6}}$$

$$Xf = \sqrt{0.25 + If}, \quad Xr = \sqrt{0.25 + Ir}$$

$$qI = -nq \cdot \left[\frac{\frac{4}{3} \cdot (Xf^2 + Xf \cdot Xr + Xr^2)}{Xf + Xr} - 1 \right]$$

$$qB = \frac{-GAMMA \cdot \sqrt{VP + PHI + 1e-6} \cdot 1}{vt} - \left[\frac{nq - 1}{nq} \right], \text{when } VGprime > 0$$

$$qB = \frac{-VGprime}{vt}, \text{when } VGprime \leq 0$$

$$qG = -qI - qB, \quad Cox = COX \cdot W \cdot L, \quad Q(I, B, D, S, G) = Cox \cdot vt \cdot q(I, B, D, S, G)$$


Symbol

 EKVLC1
 L=10e-6
 W=10e-6
 VTO=0.5
 GAMMA=0.7
 PHI=0.5
 KP=50e-6
 THETA=50e-3
 Temp=26.85
 COX=3.45e-3
 Xpart=0.6

Model


D11
 
$$I1=1+GAMMA/(2*sqrt(V2+PHI+1e-6)) \\ I2=0$$





D12

$$I1=sqrt(0.25+V2) \\ I2=0$$

 

D13

$$I1=sqrt(0.25+V2) \\ I2=0$$

  

Equation

$$Eqn1$$

$$Spart=1-Xpart$$

$$Qox=COX*W*L*vt(T2)$$

D17

$$I1=0$$

$$Q1=Xpart*V6*Qox$$


$$Q2=Spart*V6*Qox$$

$$Q3=Xpart*V5*Qox$$

$$Q4=Spart*V5*Qox$$

$$I5=0$$

$$I6=V6$$

 

D17

$$I1=0$$

$$Q1=Xpart*V6*Qox$$


$$Q2=Spart*V6*Qox$$

$$Q3=Xpart*V5*Qox$$

$$Q4=Spart*V5*Qox$$

$$I5=0$$

$$I6=V6$$

 

Compact Device Modelling 3: Building a Qucs EDD/Verilog-A model; part 3 – Verilog-A model code


Verilog-A code derived from Qucs EDD model

```
`include "disciplines.vams"
`include "constants.vams"
module EKVLC(drain, gate, source, bulk);
inout drain, gate, source, bulk;
electrical drain, gate, source, bulk;
`define attr(txt) (*txt*)
parameter real L=1e-6 from [1e-20 :inf] `attr(info="Channel length");
//
//
real VGprime,VP, n, BETA, X1, If, X2, Ir, Ispecific, Ids;
real nq, XF, Xr, qI, qB,qG;
analog begin
@(initial_model) begin
    Spart=1-Xpart; Qox=COX*W*L; T2=Temp+273.15; vt=`P_K*T2/`P_Q;
end
Vg=V(gate)-V(bulk); Vs=V(source)-V(bulk); Vd=V(drain)-V(bulk);
VGprime=Vg-VTO+PHI+GAMMA*sqrt(PHI);
VP=VGprime-PHI-GAMMA*(sqrt(VGprime+(GAMMA/2)^2)-GAMMA/2);
n=1+GAMMA/(2*sqrt(VP+PHI+4*vt));
BETA=KP*(W/L)*1/(1+THETA*VP);
X1=(VP-Vd)/vt; If=ln(1+limexp(X1/2))^2;
X2=(VP-Vs)/vt; Ir=ln(1+limexp(X2/2))^2;
Ispecific=2*n*BETA*vt*vt;
Ids=Ispecific*(If-Ir);
I(drain,source) <+ Ids;
nq=1+GAMMA/(2*sqrt(VP+PHI+1e-6));
Xf=sqrt(0.25+If); Xr=sqrt(0.25+Ir)
qI=-nq*( (4/3)*(Xf^2+Xr*Xf+Xr^2)/(Xf+Xr)^2 -1);
if (VGprime > 0)
    qB=-GAMMA*sqrt(VP+PHI+1e-6);
else qB=-VGprime/vt;
qG=-qI-qB;
I(gate, drain)<+ddt(Xpart*qG*Qox;
I(gate, source)<+ddt(Spart*qG*Qox);
I(drain, bulk)<+ddt(Xpart*qB*Qox);
I(source, bulk)<+ddt(Spart*qB*Qox);
end
endmodule
```






Compact Device Modelling 3: Building a Qucs EDD/Verilog-A model; part 4 – model test circuits and typical simulation results

Interactive testing and parameter extraction

 

SW1
Sim=SW2
Type=lin
Param=Vgs
Start=0
Stop=3
Points=7

   
SW2
Sim=DC1
Type=lin
Param=Vds
Start=0
Stop=5
Points=51





EKVL_{C1}
L=10e-6
W=10e-6
VTO=0.5
GAMMA=0.7
PHI=0.5
KP=50e-6
THETA=50e-3
Temp=26.85
COX=3.45e-3
Xpart=0.6

Equation

 Eqn1
L=10e-6
W=10e-6
COX=3.45e-3
Cg_norm=COX*W*L
Omega=2*pi*frequency
Y=stoy(S)
Cg=imag(Y[1,1]/Omega)
Cg_2D_plot=PlotVs(Cg/Cg_norm,Vgs)
Cg_3D_plot=PlotVs(Cg/Cg_norm,Vds, Vgs)
Cg_a=PlotVs(Cg,Vgs)



  Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 1



Qucs project:
MAPPEExamples_prj
↓
Startup_MAPP.m
vsrsrcRLC_transient_demo.m
..
..

This is the Berkeley Model and Algorithm Prototyping Platform (MAPP)
- git branch 2014-12-10-alpha-release
- git version MAPP-alpha-v1.00.01
- installed under:
`/home/mike/MAPP-alpha-v1.00.01.`

MAPP paths have been set up.

type "help MAPP" (without the quotes) to start.

octave:3>

MAPP code in Qucs edit window

```
%vsrcRCL_transient_demo.m
%
% To start this transient demo simulation,
% enter Octave script name vsrcRCL_transient_demo
% in the Qucs Octave command window.

clear;
RCLcktnet.cktname = 'RCL transient demo circuit';
RCLcktnet.nodenames = {'n1', 'n2', 'n3'}; % non-ground nodes
RCLcktnet.groundnode = 'gnd';

RCLcktnet = add_element(RCLcktnet, resModSpec(), 'R1', {'n1', 'n2'});
RCLcktnet = add_element(RCLcktnet, capModSpec(), 'C1', {'n2', 'n3'});
RCLcktnet = add_element(RCLcktnet, indModSpec(), 'L1', {'n3', 'n1'});

VinDC = 0.0;
Vtran = @(t, args) args.A*sin(2*pi*args.f*t + args.phi);
Vargs.A = 1; Vargs.f = 1e5; Vargs.phi = 0;
RCLcktnet = add_element(RCLcktnet, vsrcModSpec, 'V1', {'n1', 'n2'});

%
% >> cktnetlist
% >> celldisp(cktnetlist.elements)

DAE = MNA_EqnEngine(RCLcktnet);
dcop = dot_op(DAE);
%
feval(dcop.print, dcop);

xinit = zeros(feval(DAE.nunks, DAE), 1); % zero-state step re
tstart = 0; tstep = 1e-7; tstop = 1.5e-5;
%TRANobj = dot_transient(DAE, xinit, tstart, tstep, tstop);
%feval(TRANobj.plot, TRANobj);
%
%4. Rerun transient simulation with a different input:
```

+

+

+

+

Output on slide 8 →


vsrsrcRCL_transient_demo0

Background to MAPP:


http://www.mos-ak.org/berkeley_2014/presentations/07_Jaijeet_Roychowdhury_MOS-AK_Berkeley_2014.pdf
http://www.mos-ak.org/berkeley_2014/presentations/07_Tianshi_Wang_MOS-AK_Berkeley_2014.pdf

Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 2

Qucs circuit schematic and output data

 

From slide 33

 


MAPP output data

Background to MAPP:

<http://draco.eecs.berkeley.edu/dracotiki/tiki-index.php?page=MAPPfeatures>


Jaijeet Roychowdhury, Numerical simulation and modelling of electronic and biochemical systems, Foundations and Trends in Electronic Design Automation 3:2-3, NOW, 2009

 Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 3



Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 4

 Qucs evaluation of tunnel diode model equations



```
function plotIV_tunnelDiode_ModSpec_wrapper()
    MOD = tunnelDiode_ModSpec_wrapper(); →
    vs = -0.05:0.001:0.4;
    is = zeros(size(vs));

    S = ee_model_parm2struct(MOD);
    for idx = 1:1:size(is,2)
        S.vpn = vs(1,idx);
        is(1,idx) = MOD.fe_of_S(S);
    end →
    figure();

    plot([min(vs), max(vs)], [0, 0], 'Color', 'red', ...
        'LineWidth', 1.25, 'LineStyle', '--');
    hold on;
    plot([0, 0], [min(is), max(is)]*1e6, 'Color', ...
        'red', 'LineWidth', 1.25, 'LineStyle', '--');
    h = plot(vs, is*1e6, 'Color', 'blue', 'LineWidth', 1.75);

    axis tight;
    box on;
    grid on;
    set(gca,'FontName','Times New Roman','FontSize',...
        15,'FontWeight','bold');
    xlabel('vpn (V)','FontName','Times New Roman',...
        'FontSize',18,'FontWeight','bold');
    ylabel('ipn (uA)','FontName','Times New Roman',...
        'FontSize',18,'FontWeight','bold');
    title(['I/V curve of a tunnel diode'],'FontName',...
        'Times New Roman','FontSize',18,'FontWeight','bold');
    set(gcf,'color','white');

end
```

MAPP tunnel diode test wrapper

Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 5


MAPP tunnel diode compact device model

```
function MOD = tunnelDiode_ModSpec_wrapper()
    MOD = ee_model();
    MOD = add_to_ee_model(MOD, 'external_nodes', {'p', 'n'});
    MOD = add_to_ee_model(MOD, 'explicit_outs', {'ipn'});
    MOD = add_to_ee_model(MOD, 'parms', {'Is', 1e-12, 'VT', 0.025});
    MOD = add_to_ee_model(MOD, 'parms', {'Ip', 1e-5, 'Vp', 0.1});
    MOD = add_to_ee_model(MOD, 'parms', {'Iv', 1e-6, 'Vv', 0.4, 'K', 5});
    MOD = add_to_ee_model(MOD, 'parms', {'C', 0});
    MOD = add_to_ee_model(MOD, 'f', @f);
    MOD = add_to_ee_model(MOD, 'q', @q);
    MOD = finish_ee_model(MOD);
end

function out = f(S)
    v2struct(S);
    I_diode = Is*(exp(vpn/VT)-1);
    I_excess = Iv * exp(K * (vpn - Vv));
    I_tunnel = (Ip/Vp) * vpn * exp(-1/Vp * (vpn - Vp));
    out = I_diode + I_tunnel + I_excess;
end

function out = q(S)
    v2struct(S);
    out = C*vpn;
end
```

Tunnel diode I/V curve

 

MAPP post-simulation output

Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 6

```
function out = plotGV_tunnelDiode_ModSpec_wrapper()
    MOD = tunnelDiode_ModSpec_wrapper();


    vs = -0.05:0.001:0.4;
    gs = zeros(size(vs));

    for idx = 1:1:size(gs,2)
        gs(1,idx) = MOD.dfe_dvecX(vs(idx), [], [], [], MOD);
    end

    figure();
    plot([min(vs), max(vs)], [0, 0], 'Color', 'red', 'LineWidth', ...
        1.25, 'LineStyle', '--');
    hold on;
    plot([0, 0], [min(gs), max(gs)], 'Color', 'red', 'LineWidth', ...
        1.25, 'LineStyle', '--');
    h = plot(vs, gs, 'Color', 'blue', 'LineWidth', 1.75);

    axis tight;
    box on;
    grid on;
    set(gca,'FontName','Times New Roman','FontSize',...
        15,'FontWeight','bold');
    xlabel('vpn (V)','FontName','Times New Roman','FontSize',...
        18,'FontWeight','bold');
    ylabel('transconductance G (S)','FontName','Times New Roman',...
        'FontSize',18,'FontWeight','bold');
    title(['G/V curve of a tunnel diode'],'FontName','Times New Roman',...
        'FontSize',18,'FontWeight','bold');
    set(gcf,'color','white');

end
```

 

Tunnel diode G/V curve

Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 7

Equation

Model_parameters

Vv=0.4

VT=0.025

Ip=1e-5

Vp=0.1

lv=1e-6

K5

Is=1e-12

Equation



Model_equations

Idiode=Is*(exp(Vpn/VT)-1.0)

Iexcess=lv*exp(K*(Vpn-Vv))


Ipn=Idiode+Iexcess+Itunnel

Itunnel=Ip*(Vpn/Vp)*exp((Vp-Vpn)/Vp)

  


Compact device modelling: 3. Expanded compact device modelling capabilities with the Berkeley Model and Algorithm Prototyping Platform (MAPP); part 8


```
// Tunnel diode Verilog-A compact device model.
// Verilog-A code translated, by hand, from
// MAPP model.
//
`include "disciplines.vams"
`include "constants.vams"
//
module TD(p,n);
inout p,n;
electrical p,n;
//
parameter Is=1e-12 from [1e-20 : inf];
parameter Ip=1e-5 from [1e-20 : inf];
parameter Iv=1e-6 from [1e-20 : inf];
parameter Vp=0.1 from [1e-20 : inf];
parameter Vv=0.4 from [1e-20 : inf];
parameter KTD = 5 from [1e-20 : inf];
parameter VT=0.025 from [1e-20 : inf];
parameter C=1e-15 from [1e-20 : inf];
//
real Idiode, Iexcess, Itunnel;
//
analog begin
Idiode = Is*(exp(V(p,n)/VT)-1.0);
Iexcess = Iv*exp(KTD*(V(p,n)-Vv));
Itunnel = Ip*(V(p,n)/Vp)*exp(Vp-V(p,n)/Vp);
I(p,n) <+ Idiode+Iexcess+Itunnel;
I(p,n) <+ ddt(C*V(p,n));
end
endmodule
```

 

 A unified GPL compact device modelling and simulation platform



 Qucs development: 1. A unified GPL compact device modelling and simulation platform; SPICE netlist synthesis



```
* Qucs 0.0.19
* Qucs 0.0.19 TD.sch
.SUBCKT TD _net0 _net1 VT=0.025 Is=1e-12 Ip=1e-5 Iv=1e-6 Vp=0.1 Vv=0.4 K=5 C=0.01p
BD1I0 _net0 _net1 I=Is*(exp((V(_net0)-V(_net1))/VT)-1.0)
GD1Q0 _net0 _net1 nD1Q0 _net1 1.0
LD1Q0 nD1Q0 _net1 1.0
BD1Q0 nD1Q0 _net1 I=-(C*(V(_net0)-V(_net1)))
BD1I1 _net0 _net1 I=lv*exp(K*((V(_net0)-V(_net1))-Vv))
BD1I2 _net0 _net1 I=Ip*((V(_net0)-V(_net1))/Vp)*exp((Vp-(V(_net0)-V(_net1)))/Vp)
.ENDS
XTD2 _net0 0 TD VT=0.025 Is=1E-12 Ip=1E-5 Iv=1E-6 Vp=0.1 Vv=0.4 K=5 C=0.01P
VI_TD1 _net1 _net0 DC 0 AC 0
VI1 _net1 0 DC 0.1
.control
set filetype=ascii
DC V1 -0.05 0.4 0.000997783
write _dc.txt VI_TD1#branch
destroy all
reset

exit
.endc
.END
```





Qucs schematic

→ Synthesis →


Ngspice/Xyce netlist



  
A unified GPL compact device modelling and simulation platform: ngspice and Xyce component symbols



 A unified GPL compact device modelling and simulation platform: Signal generator test examples



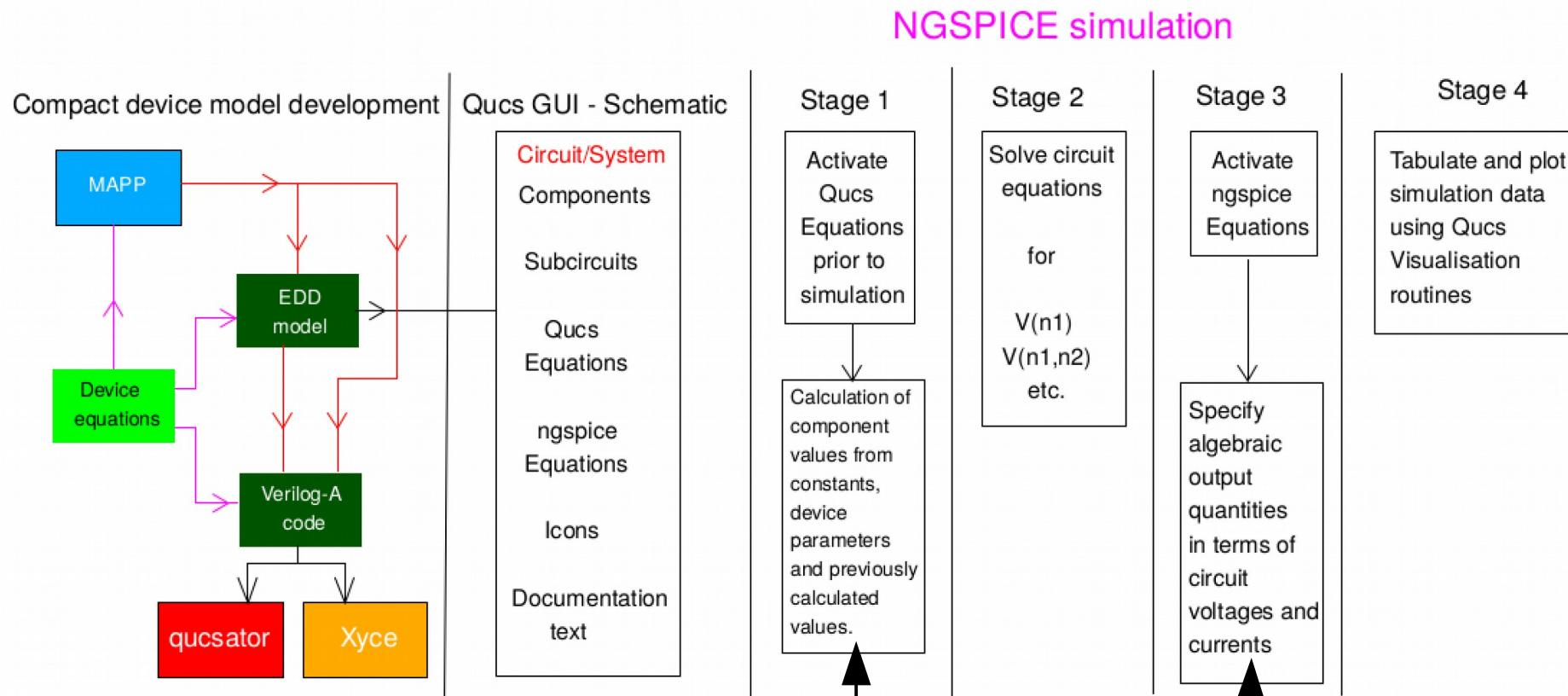A unified GPL compact device modelling and simulation platform: Integrating Qucs and ngspice



Ngspice/ngnutmeg

Stores data in the form of vectors: time, voltage etc. Each type of vector can be operated on and combined algebraically. Expressions are algebraic formula involving vectors and scalars.

Ngnutmeg defines the following functions: mag, ph, cph, j, real, imag, db, log, ln, exp, abs, sqrt, sin, cos, tan, atan, sinh, cosh, tanh, floor, ceil, norm, mean avg, group_delay, vector, unitvector, length, interpolate, deriv, vecd, vecmax, rnd, sgauss, sunif, poisson, exponential.

Allowed operators: +, -, *, /, ^, %, ., , >, <, >=, <=, <>, &, |, !, =

Constants: pi, e, c, I, kelvin, echarge, boltz, plank, yes, no, TRUE, FALSE

A unified GPL compact device modelling and simulation platform: Typical simulation examples


Z1

Z=mesfet model



Z Line 2=.model mesfet model nmf level = 1 vto=-2 beta = 3e-3 alpha = 2

Z Line 3=+ lambda = 0.02 cgd = 0.2e-12 cgs = 1e-12

 Z Line 4=+ Rd = 1.3 Rs = 1.3 B = 0.3 PB = 0.6




  **(1) MESFET DC characteristic test bench
using nested parameter sweep**



 **(2) Basic full wave rectifier with transformer
modelled by SPICE K type inductive
coupling**

A unified GPL compact device modelling and simulation platform: Semiconductor diode Cd and Rd extraction using Y parameters



ac simulation


AC1
Type=lin
Start=10MHz
Stop=10.1 MHz
Points=1

Parameter sweep


SW1
Sim=AC1
Type=lin
Param=V1
Start=0
Stop=0.8
Points=21

Nutmeg


 
NutmegEq1
Simulation=ac
y=1
Freq=10e6
Omega=2*pi*Freq
Yd_imag=imag(VPr1#branch/V(n3))
Cd=Yd_imag/Omega
Rd=1/real(VPr1#branch/V(n3))



 
A unified GPL compact device modelling and simulation platform: More ngspice simulation types; small signal distortion



Equation	Nutmeg	transient simulation	Distortion simulation	dc simulation
Eqn1	NutmegEq1	TR1	DISTO1	DC1
Rload=47k	Simulation=disto	Type=lin	Type=lin	
K=out.v/in.v	H2=disto1.v(out)	Start=0	Start=1 Hz	
	H3=disto2.v(out)	Stop=1 ms	Stop=10 kHz	
			Points=1000	

  


 A unified GPL compact device modelling and simulation platform: More ngspice simulation types; Fourier analysis




A unified GPL compact device modelling and simulation platform: More ngspice simulation types; Noise analysis

Large signal transient noise

 


Small signal AC noise

 

Parameter sweep

Noise simulation




noise.R5	BJT-noise_ngspice:noise_total	BJT-noise_ngspice:onoise_total
1e3	1.28e-10	4.58e-10
1.45e3	1.15e-10	8.09e-10
1.9e3	1.08e-10	1.21e-09
2.35e3	1.04e-10	1.64e-09
2.8e3	1.01e-10	2.09e-09
3.25e3	9.88e-11	2.53e-09
3.7e3	9.72e-11	2.97e-09
4.15e3	9.6e-11	3.4e-09

 


A unified GPL compact device modelling and simulation platform: More ngspice simulation types; Custom ngspice simulation

Ngspice custom simulation

```
CUSTOM1
SpiceCode=
** Extraction of diode Cd and Rd values for 0 <= Vd <=0.9 V DC.
*****
* Initialise data
destroy all
set filetype=ascii
let count = 0
let count_Fin = 90
*****
** Run simulation and extract Cd and Rd values for each value of V2 DC.
while count le count_Fin
  alter V2 = count*0.01
  ac lin 1 1e4 2e4
  let Omega = 2*pi*frequency
  let Cd = imag(VPr1#branch/V(Nd))/Omega
  let Rd = 1.0/(real( VPr1#branch/V(Nd))+1e-15 )
  write Y11Test_ac.txt Cd Rd VPr1#branch V(Nd)
  set appendwrite
  let count=count+1
end
*****
```

   

 A unified GPL compact device modelling and simulation platform: More ngspice simulation types; Monte Carlo analysis





Ngspice
custom simulation

```
CUSTOM1
SpiceCode=
set filetype=ascii
let mc_runs = 5
let run = 0

define unif(nom, rvar) (nom + (nom*rvar) * sunif(0))
define aunif(nom, avar) (nom + avar * sunif(0))
define gauss(nom, rvar, sig) (nom + (nom*rvar)/sig * sgauss(0))
define agauss(nom, avar, sig) (nom + avar/sig * sgauss(0))
* define limit(nom, avar) (nom + ((sgauss(0) ge 0) ? avar : -avar))
define limit(nom, avar) (nom + ((sgauss(0) >= 0) ? avar : -avar))
*
dowhile run < mc_runs $ loop starts here
*
* alter c1 = unif(1e-09, 0.1)
* alter c1 = aunif(1e-09, 100e-12)
* alter c1 = gauss(1e-09, 0.1, 3)
* alter c1 = agauss(1e-09, 100e-12, 3)
*
alter c1 = unif(1e-09, 0.1)
alter l1 = unif(10e-06, 0.1)
alter c2 = unif(1e-09, 0.1)
alter l2 = unif(10e-06, 0.1)
alter l3 = unif(40e-06, 0.1)
alter c3 = limit(250e-12, 25e-12)
*
ac oct 100 250K 10Meg

set run ="$&run" $ create a variable from the vector

  let K = db(v(out))
write MonteCarlo1_custom.txt v(out) K
set appendwrite
let run = run + 1
end $ loop ends here
```



Summary

This presentation outlined the compact modelling and simulation features implemented in the current and next generation versions of the Qucs GPL circuit simulation tool set.

Qucs version 0.0.19 will be released on, or before, 1 September 2015.

The latest Qucs development version can be downloaded using git from <https://github.com/Qucs/qucs/>

If you wish to follow the development of Qucs see the regularly updated spice4qucs-help document at <http://qucs-help.readthedocs.org/en/spice4qucs/DModel.html>

Beyond Qucs-0.0.19

- Addition of SPICE .PZ etc to Qucs
- Improvements in Qucs/Xyce link
- Synthesis of SPICE code for Qucs RFEDD models
- Improved RF device modelling and simulation
- Synthesis of Verilog-A model code from Qucs EDD compact device models
- More work on the Qucs/MAPP link

Acknowledgement: My thanks to all the members of the Qucs Development Team for their input and support during the recent intense software development phase. 53

References

- Brinson M. and Jahn S., Interactive compact device modelling using Qucs equation defined devices, International Journal of Numerical Modelling: Electrical Networks, Devices and Fields, 21(5) pp. 335-349, September/October 2008. DOI : 10.1002/jnm.676.
- Brinson M. and Jahn S., Qucs: A GPL software package for circuit simulation, compact device modelling and circuit macromodelling from DC to RF and Beyond, International Journal of Numerical Modelling: Electrical Networks, Devices and Fields, 22(4) pp. 297-319, July/August 2009. DOI : 10.1002/jnm.702.
- Brinson M. and Jahn S., Compact macromodelling of operational amplifiers with equation defined devices, International Journal of Electronics, 96(2), pp. 109-122, February 2009, DOI:10.1080/00207210802580288, ISSN :0020-7217.
- Brinson M. and Jahn S., Modelling of high-frequency inductance with Qucs non-linear radio frequency equation-defined devices, International Journal of Electronics, 96(3), March 2009, DOI:10.1080/00207210802640603, ISSN : 0020-7217.
- Brinson M.E., Jahn S. and Nabijou H., Z Domain delay subcircuits and compact Verilog-A macromodels for mixed-mode sampled data circuit simulation, Test Technology Technical Council (TTTC) of the IEEE Computer Society, Radioelectronics & Informatics Journal, Vol. 45, No. 2, pp. 14-20, April/June 2009. ISSN 1563-0064.
- Brinson M.E. and Nabijou H., Adaptive subcircuits and compact Verilog-A macromodels as integrated design and analysis blocks in Qucs circuit simulation, International Journal of Electronics, Vol. 98 (5), pp. 631-645, May 2011. DOI: 10.1080/00207217.2011.562452.
- Brinson M.E., Jahn S. and Nabijou H., A tabular source approach to modelling and simulating device and circuit noise in the time domain, International Journal of Numerical Modelling: Electronic Networks, Devices and Fields, Vol 26(6), pp. 555-567, November/December 2011. DOI: 10.1002/jnm801.
- Brinson M. and Jahn S., Compact device modelling for established and emerging technologies with the Qucs GPL circuit simulator, Mixed design of Integrated Circuits and Systems (MIXDES) 2009, Proceedings of the 16 International Conference, pp. 39-44, Lodz, Poland, June 2009. ISBN 978-1-4244-4798-5. INSPEC Accession Number: 10928855. Available from: <http://ieeexplore.org> .



References

- Brinson M.E. and Nabijou H., Adaptive EPFL-EKV long and short channel MOS device models for Qucs, SPICE and Modelica circuit simulation, Mixed design of Integrated Circuits and Systems (MIXDES) 2011, Proceedings of the 18 International Conference, pp. 65-70, Gliwice, Poland, June 2011, ISBN 978-1-4577-0804-1, INSPEC Accession Number: 12219696. Available from <http://ieeexplore.org> .
- Brinson M.E. and Margraf M., Verilog-A compact semiconductor device modelling and circuit macromodelling with the QucsStudio-ADMS “Turn-Key” modelling system , Mixed design of Integrated Circuits and Systems (MIXDES) 2012, Proceedings of the 19 International Conference, pp. 65-70, Warsaw, Poland, May 2011. ISBN 978-83-62954-43-8, INSPEC Accession Number: 12219696. Available from <http://ieeexplore.org>
- Brinson M.E. From Qucs to QucsStudio: An international project to develop a freely available GU Public Licence circuit simulator with compact device modelling tools, data processing capabilities, manufacturing features and an analogue/RF design environment for engineers, MOS-AK/GSA International workshop on Device modeling for Microsystems, Jaypee Institute of Information Technology, Nodia, March 2012. Available from: http://www.mos-ak.org/india/presentations/Brinson_MOS-AK_India12.pdf .
- Brinson M.E., Jahn S. and Nabijou H., A hybrid Verilog-A and equation-defined subcircuit approach to MOS switched current analog cell simulation, IETE Journal of research, Vol 58(3), pp. 177=185, May-June 2012.
- Mike E. Brinson, and Hassan Nabijou, Adaptive EPFL-EKV long and short channel MOS device models for Qucs, SPICE and Modelica circuit simulation, International Journal of microelectronics and Computer Science, Vol.3, NO. 1, 2012, pp. 1-6. ISSN 2080-8755.
- Mike E. Brinson, and Michael Margraf, Verilog-A compact semiconductor device modelling and circuit macromodelling with the QucsStudio-ADMS “Turn-Key” modelling system, International Journal of microelectronics and Computer Science, Vol.3, NO. 1, 2012, pp. 32-40. ISSN 2080-8755.

References

Brinson M.E., Jahn S. and Nabijou H., A hybrid Verilog-A and equation-defined subcircuit approach to MOS switched current analog cell modeling and simulation in the transient and large signal AC domains, Mixed design of Integrated Circuits and Systems (MIXDES) 2010, Proceedings of the 17 International Conference, pp. 3-48, Wroclaw, Poland, June 2010. ISBN 978-1-4244-7011-2, INSPEC Accession Number: 11487844. Available from: http://ieeexplore.ieee.org/xpl/freeabs_all.jsp?arnumber=5551306

Brinson M.E., Jahn S. and Nabijou H., Adaptive EPFL-EKV long and short channel MOS device models for Qucs, SPICE and Modelica circuit simulation, Mixed design of Integrated Circuits and Systems (MIXDES) 2011, Proceedings of the 18 International Conference, pp. 65-70, Gliwice, Poland, June 2011. ISBN 978-1-4577-0304-1. INSPEC Accession Number: 12219696. Available from http://ieeexplore.ieee.org/xpl/freeabs_all.jsp?arnumber=6016035

Jahn S., Brinson M.E., Margraf M., Parruitte H., Ardouin B., Nenzi P., and Lemaitre L., GNU simulators supporting Verilog-A compact model standardization, MOS-AK International Meeting, Premstaetten, Germany, March 2007. Available from: http://www.mos-ak.org/premstaetten/papers/MOS-AK_QUCS_ngspice_ADMS.pdf

Brinson M. and Jahn S., Building device models and circuit macromodels with the Qucs GPL simulator : A demonstration, Presentation to the European Network on Compact Modelling (COMON), Frankfurt(O), Germany, 2 April 2009. Available from: http://www.mos-ak.org/frankfurt_o/papers/M_Brinson_Qucs_COMON_April_2_2009_final.pdf

Brinson M., Jahn S. and Cullinan M., Advances in compact semiconductor device modelling and circuit macromodelling with the Qucs GPL circuit simulator, MOS-AK International Meeting, Frankfurt(O), Germany, 3 April 2009. Available from: http://www.mos-ak.org/frankfurt_o/papers/P_7_Brinson_MOS-AK_April_2009_final.pdf

Brinson M.E., Jahn S. and Nabijou H., Qucs, SPICE and Modelica equation-defined modelling techniques for the construction of compact device models based on a common model template structure, MOS-AK/GSA International workshop on the frontiers of compact modeling for advanced analog/RF applications, Université Pierre et Marie Curie, Paris, April 2011. Available from: http://www.mos-ak.org/paris/papers/P06_Brinson_MOS-AK_Paris.pdf

References

- Brinson M.E. and Nabijou H., Adaptive EPFL-EKV long and short channel MOS device models for Qucs, SPICE and Modelica circuit simulation, Mixed design of Integrated Circuits and Systems (MIXDES) 2011, Proceedings of the 18 International Conference, pp. 65-70, Gliwice, Poland, June 2011, ISBN 978-1-4577-0804-1, INSPEC Accession Number: 12219696. Available from <http://ieeexplore.org> .
- Brinson M.E. and Margraf M., Verilog-A compact semiconductor device modelling and circuit macromodelling with the QucsStudio-ADMS “Turn-Key” modelling system , Mixed design of Integrated Circuits and Systems (MIXDES) 2012, Proceedings of the 19 International Conference, pp. 65-70, Warsaw, Poland, May 2011. ISBN 978-83-62954-43-8, INSPEC Accession Number: 12219696. Available from <http://ieeexplore.org>
- Brinson M.E. From Qucs to QucsStudio: An international project to develop a freely available GU Public Licence circuit simulator with compact device modelling tools, data processing capabilities, manufacturing features and an analogue/RF design environment for engineers, MOS-AK/GSA International workshop on Device modeling for Microsystems, Jaypee Institute of Information Technology, Nodia, March 2012. Available from: http://www.mos-ak.org/india/presentations/Brinson_MOS-AK_India12.pdf .
- Brinson M.E., Jahn S. and Nabijou H., A hybrid Verilog-A and equation-defined subcircuit approach to MOS switched current analog cell simulation, IETE Journal of research, Vol 58(3), pp. 177=185, May-June 2012.
- Mike E. Brinson, and Hassan Nabijou, Adaptive EPFL-EKV long and short channel MOS device models for Qucs, SPICE and Modelica circuit simulation, International Journal of microelectronics and Computer Science, Vol.3, NO. 1, 2012, pp. 1-6. ISSN 2080-8755.
- Mike E. Brinson, and Michael Margraf, Verilog-A compact semiconductor device modelling and circuit macromodelling with the QucsStudio-ADMS “Turn-Key” modelling system, International Journal of microelectronics and Computer Science, Vol.3, NO. 1, 2012, pp. 32-40. ISSN 2080-8755.

References

Mike Brinson, Richard Crozier, Clemens Novak, Bastien Roucaries, Frans Schreuder, Guilherme Brondani Torri, Building a second generation Qucs GPL circuit simulator: package structure, simulation features and compact device modelling capabilities, MOS-AK Compact Device Modelling Workshop, London Metropolitan University, London(UK), March 28-29, 2014. Available from:

http://www.mos-ak.org/london_2014/presentations/09_Mike_Brinson_MOS-AK_London_2014.pdf

Mike Brinson, Richard Crozier, Clemens Novak, Bastien Roucaries, Frans Schreuder, Guilherme Brondani Torri, QUCS Roadmap: background to the new features in release 0.0.18 and an outline of future software development directions, 12th MOS-AK ESSDERC/ESSCIRC Workshop, Venice(IT), September 26, 2014. Available from:

http://www.mos-ak.org/venice_2014/publications/T_4_Brinson_MOS-AK_Venice_2014.pdf

Mike Brinson, Richard Crozier, Clemens Novak, Bastien Roucaries, Frans Schreuder, Guilherme B. Torri, W. Grabinski, QUCS/ADMS/Verilog-A Update, 7th International MOS-AK at UC Berkeley (US), Dec.12, 2014. Available from:

http://www.mos-ak.org/berkeley_2014/presentations/04_Wladek_Grabinski_MOS-AK_Berkeley_2014.pdf

Mike Brinson, Richard Crozier, Vadim Kuznetsov, Clemens Novak, Bastien Roucaries, Frans Schreuder, Guilherme Brondani Torri, Qucs: improvements and new directions in the GPL compact device modelling and circuit simulation tool, MOS-AK Workshop at DATE Grenoble (F), April 2015. Available from:

http://www.mos-ak.org/grenoble_2015/presentations/T4_Brinson_MOS-AK_Grenoble_2015.pdf

Grabinski W, Brinson M, Nenzi P, Lannutti F, Makris N, Antonopoulos A, Bucher M. Open-source circuit simulation tools for RF compact semiconductor device modelling. Invited paper. International Journal of Numerical Modelling: Electronic Networks, Devices and Fields Volume 27, Issue 5-6, September-December 2014, Pages: 761–779.
DOI: 10.1002/jnm.1973.

NEW BOOK: Open Source/GNU CAD for Compact Modelling, Editors: Wladek Grabinski and Daniel Tomaszewski. Publisher: Mark de Jongh [Mark.de.Jongh@springer.sbm.com], www.springer-sbm.com. Chapter 5: M.E. Brinson, Schematic entry and circuit simulation with Qucs. Chapter 6: M.E. Brinson, Qucs modelling and simulation of analogue/RF devices and circuits.

Qucs is a Project of the Week on SourceForge: see
<http://sourceforge.net/blog/project-of-the-week-june-1-2015/>

